

Design and Simulation of NPN and PNP BJT Overvoltage Protection Circuits

1 Introduction

Overvoltage protection is crucial in safeguarding electronic circuits from potentially damaging voltage spikes. Bipolar Junction Transistors (BJTs) are widely used in these circuits due to their fast switching characteristics and ability to handle high currents. This report explores the design and simulation of overvoltage protection circuits using NPN and PNP BJTs. The aim is to compare the behavior of these circuits and highlight their respective advantages and limitations.

2 Circuit Design

2.1 NPN BJT Overvoltage Protection Circuit

The NPN BJT overvoltage protection circuit is designed to protect the load from excessive voltage by diverting the excess voltage through the transistor when a certain threshold is exceeded. In this circuit:

- $R1$ and $R2$ are biasing resistors.
- $D2$ is a Zener diode that sets the voltage reference and provides more stability by clamping the voltage at a specific level.
- $Q1$ is the NPN BJT that acts as a switch, turning on when the voltage exceeds the Zener diode's breakdown voltage.

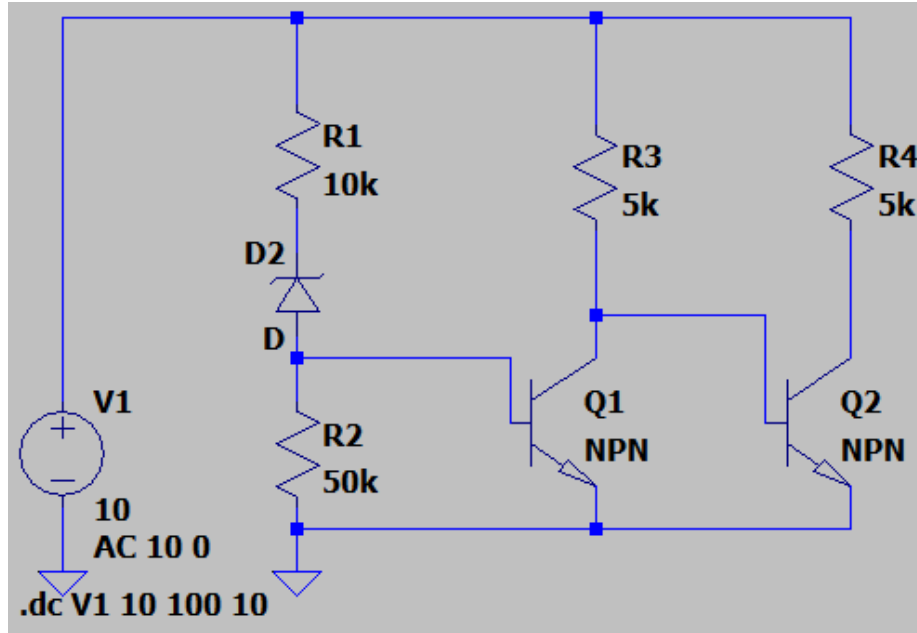


Figure 1: NPN BJT Overvoltage Protection Circuit

2.2 PNP BJT Overvoltage Protection Circuit

The PNP BJT overvoltage protection circuit operates similarly to the NPN circuit but with key differences due to the PNP transistor's characteristics. In this circuit:

- $R1$ and $R3$ are used to set the base biasing.
- $D1$ and $D2$ are diodes used for voltage reference and protection, where $D2$ (a Zener diode) provides stability by clamping the voltage.
- $Q1$ and $Q3$ are PNP BJTs that control the voltage passing through the circuit.

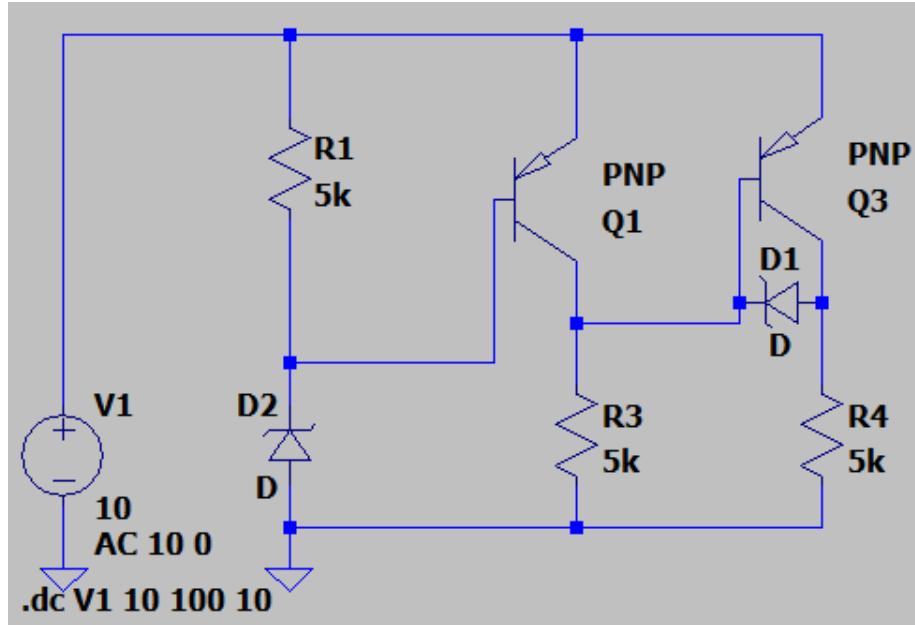


Figure 2: PNP BJT Overvoltage Protection Circuit

3 Simulation Setup

Both circuits were simulated in LTspice with the following setup:

- A DC sweep was performed with the source voltage $V1$ ranging from 10V to 100V.
- The objective was to observe the output voltage across the load as the input voltage increases, identifying how the circuits respond to overvoltage conditions.

4 Simulation Results

4.1 NPN BJT Circuit Simulation Results

The output voltage across the load in the NPN circuit decreases as the input voltage increases, indicating that the NPN transistor is effectively shunting the excess voltage once it exceeds the Zener diode's breakdown voltage.

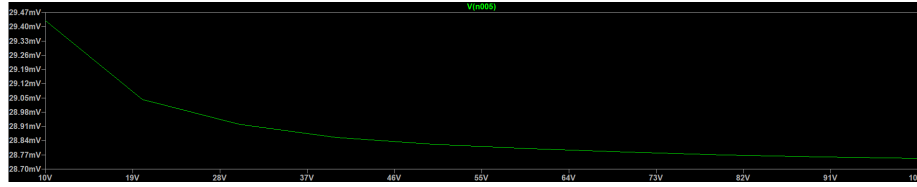


Figure 3: NPN Circuit Output Voltage vs. Input Voltage

4.2 PNP BJT Circuit Simulation Results

In contrast to the NPN circuit, the output voltage in the PNP circuit shows a linear increase with the input voltage. This behavior is due to the PNP transistor's operation, where it provides a linear control over the voltage passing through the load as the input voltage rises.



Figure 4: PNP Circuit Output Voltage vs. Input Voltage

5 Comparison and Discussion

The simulation results reveal distinct differences in the behavior of NPN and PNP overvoltage protection circuits:

- **NPN Circuit:** The output voltage decreases as the input voltage increases, effectively protecting the load from overvoltage.
- **PNP Circuit:** The output voltage increases linearly with the input voltage, indicating a more controlled but less protective behavior under increasing input voltage conditions.

The choice between NPN and PNP BJTs for overvoltage protection depends on the specific requirements of the application. NPN circuits offer better protection by shunting excess voltage, whereas PNP circuits provide linear voltage control.

6 Conclusion

The NPN and PNP BJT overvoltage protection circuits exhibit different behaviors in response to increasing input voltages. NPN circuits are better suited

for applications requiring strict overvoltage protection, while PNP circuits may be used where linear voltage control is desired. Future work could explore optimizing these circuits for specific use cases, considering factors such as power dissipation, response time, and load requirements.